

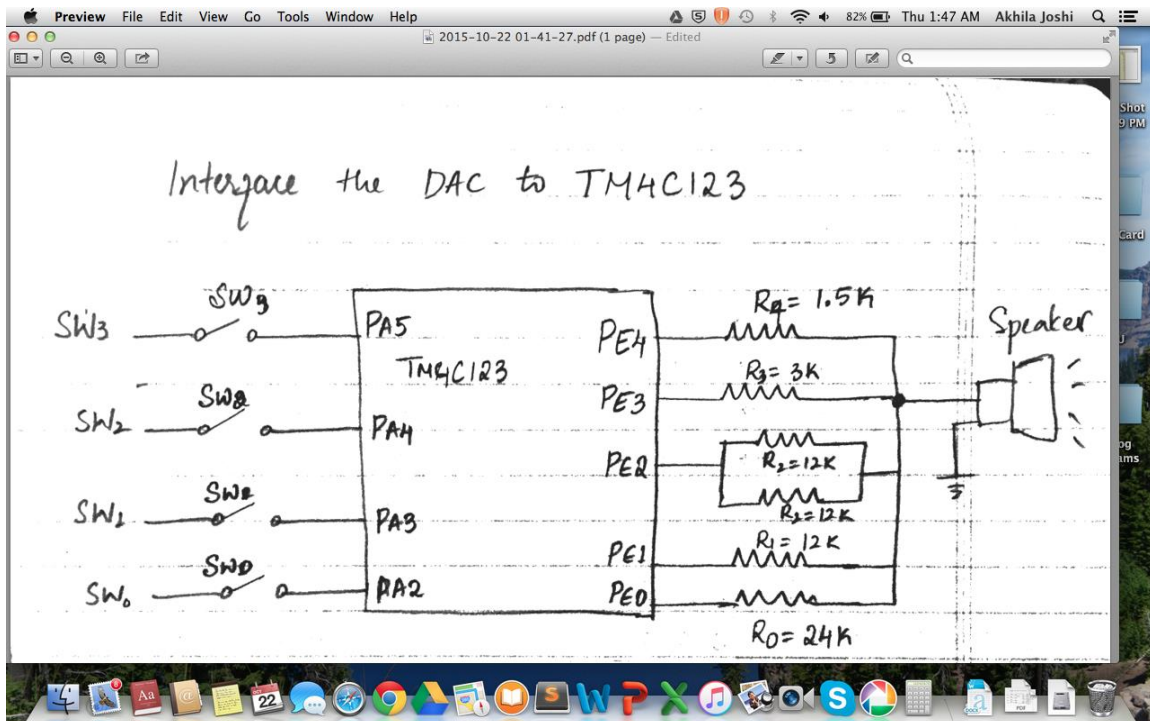


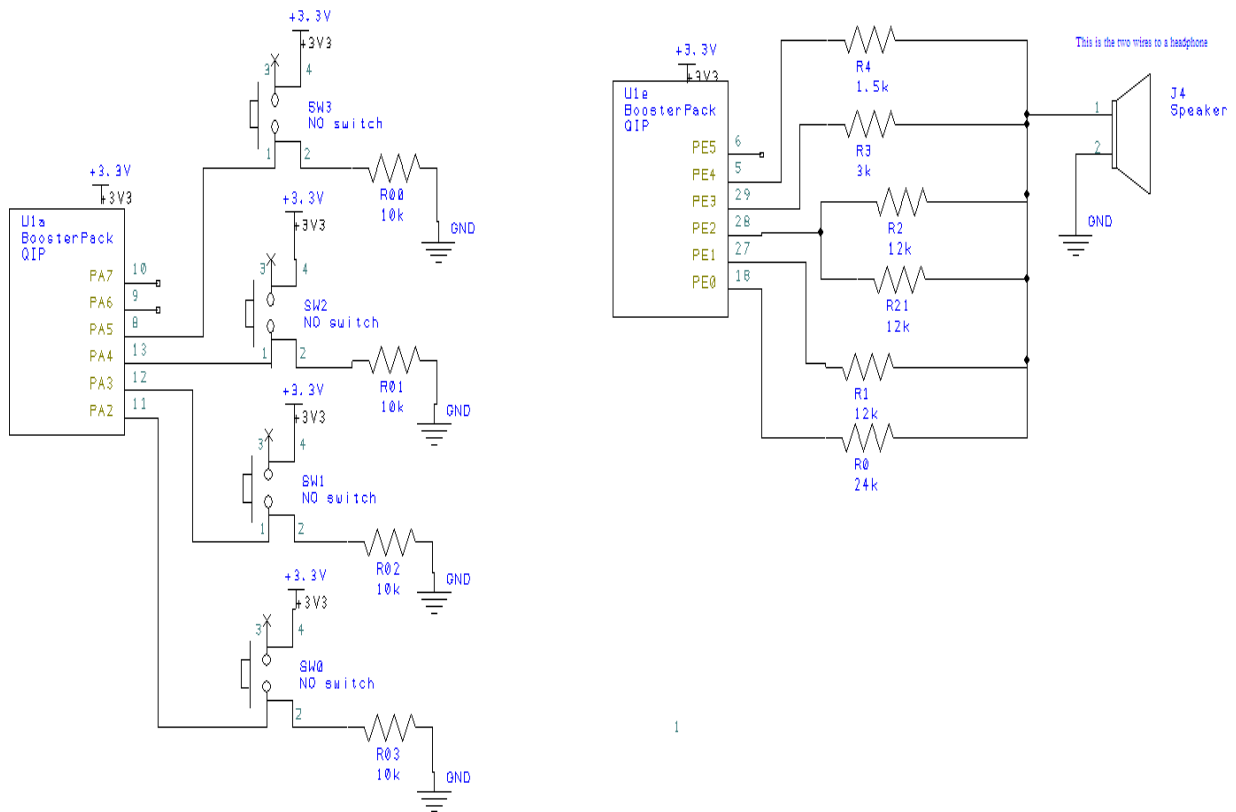Circuit required to Interface the DAC to the TM4C123.



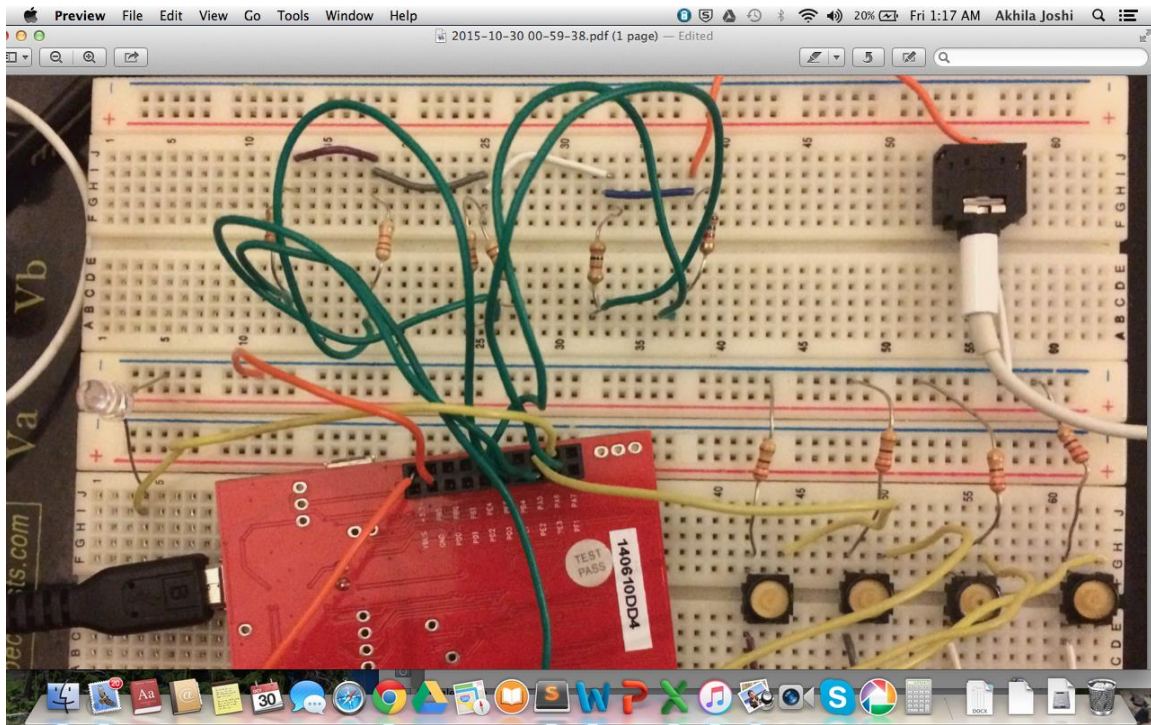

This image shows the DAC output and Piano input connection on Bread Board. Switches and DAC connections were made using PCB artist circuit connection.